

Bihar Engineering University, Patna

End Semester Examination -2023

Course: B.Tech

Semester: IV

Time: 03 Hours

Code: 110401

Subject: Analog Electronics

Full Marks: 70


Instructions:-

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

Q.1 Choose the correct answer of the following (any seven Question only):

[2 x 7 = 14]

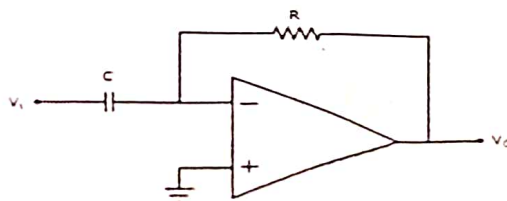- (a) The resistance in hybrid- π model is used for
 - (i) Analysis of BJT at high frequency
 - (ii) analysis of BJT at low frequency
 - (iii) Analysis of BJT for feedback
 - (iv) analysis of BJT for large signal
- (b) Diode is a device
 - (i) Unidirectional
 - (ii) Bidirectional
 - (iii) Non-linear
 - (iv) both a & c
- (c) How is the transconductance at saturation related to the pinch off voltage of the JFET?
 - (i) Inversely proportional
 - (ii) Directly proportional
 - (iii) Inverse-squarely related
 - (iv) Directly and proportional to square of the pinch-off voltage
- (d) A Ripple factor of half wave rectifier is _____
 - (i) 1.414
 - (ii) 1.21
 - (iii) 1.3
 - (iv) 0.48
- (e) The overall gain of multiple amplifiers in cascade can be expressed as _____ (A1, A2, A3 are individual gains)
 - (i) $A1-A2-A3$
 - (ii) $A1+A2+A3$
 - (iii) $A1/A2 \cdot A3$
 - (iv) $A1 \cdot A2 \cdot A3$
- (f) In an ideal op-amp, which is not true?
 - (i) Open loop voltage gain is infinite
 - (ii) Input resistance is infinite
 - (iii) Slew rate is infinite
 - (iv) CMRR is zero
- (g) The ratio that quantifies the device's ability to reject the common mode signals is called _____.
 - (i) Common mode rejection ratio
 - (ii) Gain ratio
 - (iii) Common mode ratio of reference
 - (iv) None of the above
- (h) What type of a device is MOSFET?
 - (i) Current-controlled
 - (ii) Voltage-controlled
 - (iii) Voltage-controlled Current source
 - (iv) Voltage-controlled Voltage source
- (i) Identify the circuit displayed below



- (i) Integrator
 (ii) Differentiator
 (iii) Adder
 (iv) Multiplier
- (j) Which of the following BJT terminal controls the current flow?


- (i) Base
 (ii) Collector
 (iii) Emitter
 (iv) Drain
- Q.2 What is PIV in diode? Derive RMS value and efficiency in half wave and full wave rectifier. [14]

- Q.3 Discuss various biasing methods used in BJT. Also write your conclusion that which biasing method is best, justify it with stability factor. [14]

- Q.4 Explain the working of depletion type MOSFET. Discuss why wedge shaped channel appears if Drain to source voltage increases at constant V_{gs} . [14]

Q.5 Determine the following

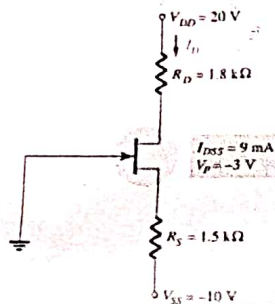- (a) I_{DQ} and V_{GSQ} [7]
 (b) V_{DS} , V_D , V_S . [7]



- Q.6 (a) Write the properties of ideal op-amp. Define CMMR, Virtual ground & slew rate. [7]
 (b) Explain inverting mode, non-inverting mode, summing amplifier and integrator circuit in op-amp. [7]

- Q.7 (a) Explain the mechanism of avalanche breakdown and zener breakdown. [7]
 (b) How signal diode is differ from zener diode. [7]

- Q.8 What is difference between active filter and passive filter? Design active low pass filter using op-amp and sketch output. [14]

Q.9 Find I_E and I_C . Assume β is very large

